

Switching Circuits Laboratory (CS29002)

Assignment 2 (21-01-2026)

- a) Design a combinational circuit that takes a 4-bit binary number $N = (A, B, C, D)$ as input, where A is the MSB and D is the LSB. The circuit produces an output F of 1 if N is a prime, and 0 otherwise. Draw the truth table of the circuit, obtain the minimized logic expression for F , and realize the circuit using basic gates.

Connect an external LED to display the value of F . *Do not use any on-board LED*. Ensure that when the LED glows, a current of about 5 mA flows through it.

- b) Design a combinational circuit that takes a BCD digit $A = (A_3, A_2, A_1, A_0)$ as input, and produces a BCD digit $B = (B_3, B_2, B_1, B_0)$ as output, where $B = (A + 4) \% 10$. Draw the truth table of the circuit, obtain logic expressions for B_3, B_2, B_1, B_0 , and realize the circuit using 2-input NAND gates only.

Display both the input and the output digits A and B on two 7-segment LED display units.

Instructions:

- 1) *For each design, draw the circuit diagram on paper, following the suggested conventions. Following this, you can issue the components and start with the realization on the breadboard.*
- 2) *After you finish each part of the experiment, show it to your assigned TA, who will be doing the evaluation.*
- 3) *Prepare a laboratory report in PDF format and upload it to Moodle by the specified deadline. A single report has to be uploaded per group.*