

## Switching Circuits Laboratory (CS29002)

### Assignment 3 (28-01-2026)

- a) Design a combinational circuit  $C$  that takes a 4-bit binary number  $B = (b_3, b_2, b_1, b_0)$  as input, and converts it to a 2-digit BCD number  $(T, U)$  as output (T – tens digit, U – units digit). For example, the input binary number '1100' will get converted to 12 ('0001 0010' in BCD).

Write the truth table for the eight bits in  $T$  and  $U$  as functions of the four bits of  $B$ . Minimize these functions using Karnaugh maps. Realize the minimized functions using NAND, NOR and NOT gates only.

Display the digits  $T$  and  $U$  on two 7-segment display units.

- b) Design an astable multivibrator  $M$  using the 555 timer IC, which generates a rectangular pulse train (clock) of: (i) frequency 50 KHz and duty cycle 90%, (ii) frequency 2 Hz and duty cycle 75%.
- c) Feed the 2 Hz clock signal as designed in (Part-b) to a 4-bit binary counter (use TTL IC 7493), and connect the outputs of the counter to the inputs of the combinational circuit  $C$  designed in (Part-a). Verify that the count values are displayed in the correct sequence.

### Instructions:

- 1) For each design, draw the circuit diagram on paper, following the suggested conventions. Following this, you can issue the components and start with the realization on the breadboard.
- 2) After you finish each part of the experiment, show it to your assigned TA, who will be doing the evaluation. There will be a penalty for late demonstration beyond the lab hours.
- 3) Prepare a laboratory report in PDF format and upload it to Moodle by the specified deadline. A single report has to be uploaded per group.