


Switching Circuits Laboratory (CS29002)

Assignment 2

January 22, 2025

1

Interfacing a LED to a TTL output

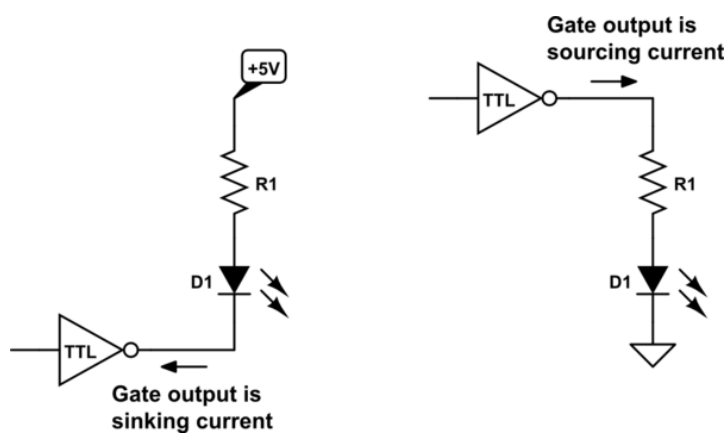

LED glows when output is 0
(recommended)

LED glows when output is 1 (not
recommended)


A TTL gate output can

- source 400 microamperes (when 1)
- sink 16 (standard) of 8 (LS family) milliamperes of current.


The voltage drop across a forward biased LED is typically 1.7 to 3.3 volts. For your calculation, assume it to be 2 volts.

2

BCD to Seven-Segment Decoder

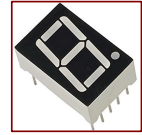

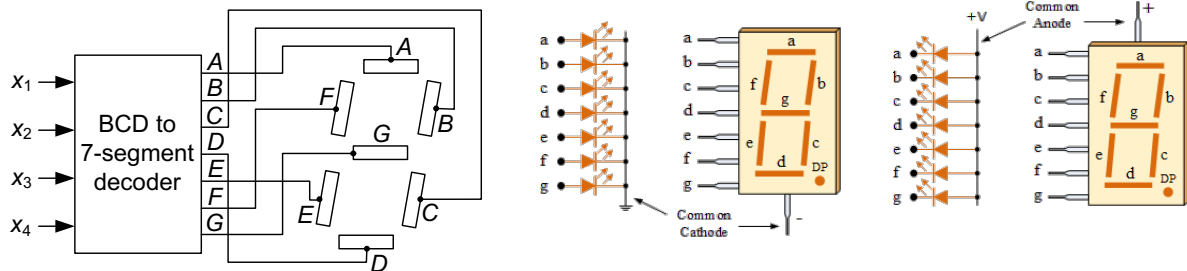- 7-segment displays are commonly used for numerical displays.
 - There are seven display segments, designed using LED, LCD, or any other technology.
 - Depending on the digit to be displayed, the appropriate segments should glow.




3

3

BCD Code

7-segment Code


Digit	x_1	x_2	x_3	x_4	A	B	C	D	E	F	G
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1

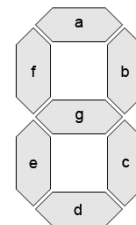


$$\begin{aligned}
 A &= x_1 + x_2'x_4' + x_2x_4 + x_3x_4 \\
 B &= x_2' + x_3'x_4' + x_3x_4 \\
 C &= x_2 + x_3' + x_4 \\
 D &= x_2'x_4' + x_2'x_3 + x_3x_4' + x_2x_3'x_4 \\
 E &= x_2'x_4' + x_3x_4' \\
 F &= x_1 + x_2x_3' + x_2x_4' + x_3'x_4' \\
 G &= x_1 + x_2'x_3 + x_2x_3' + x_3x_4'
 \end{aligned}$$

4

4

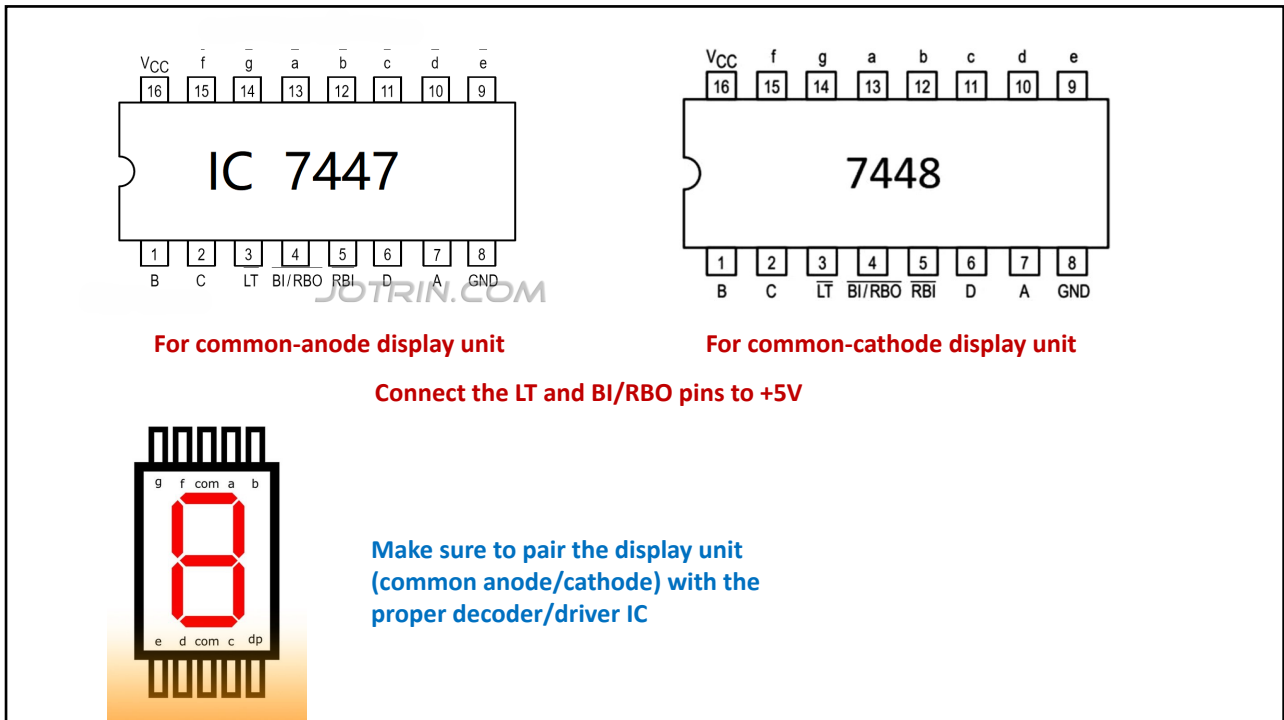

5

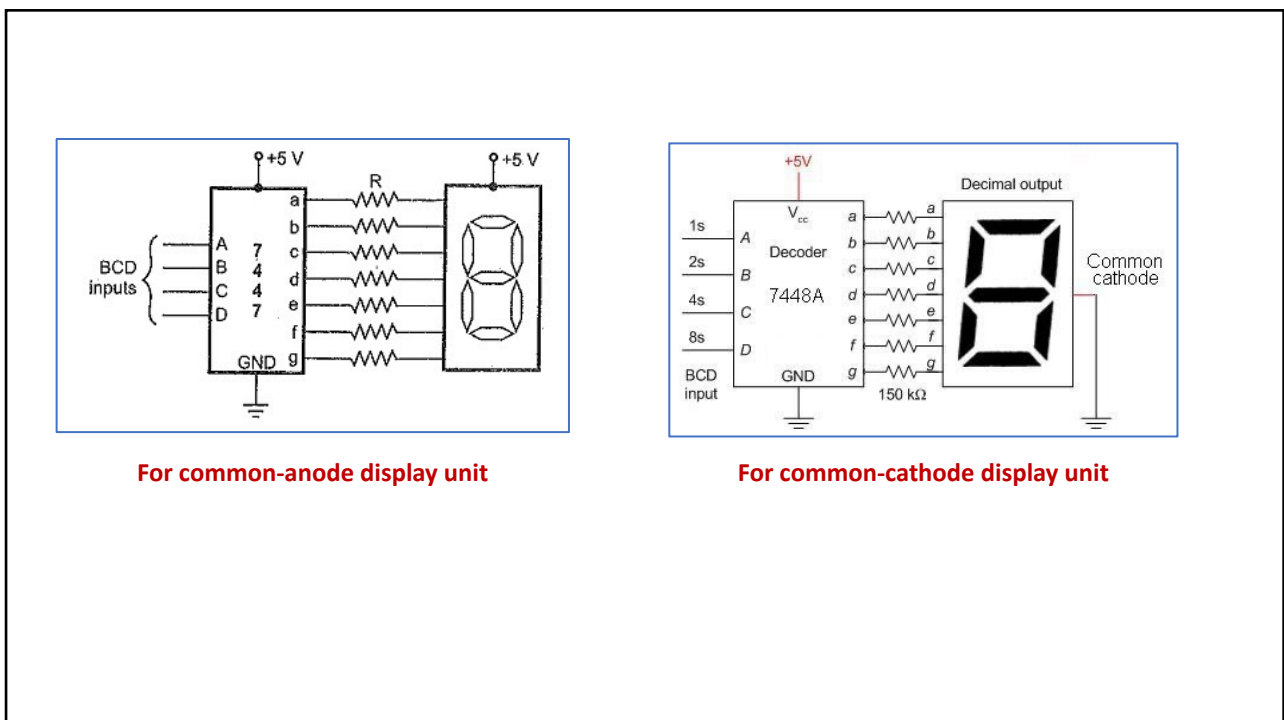

6